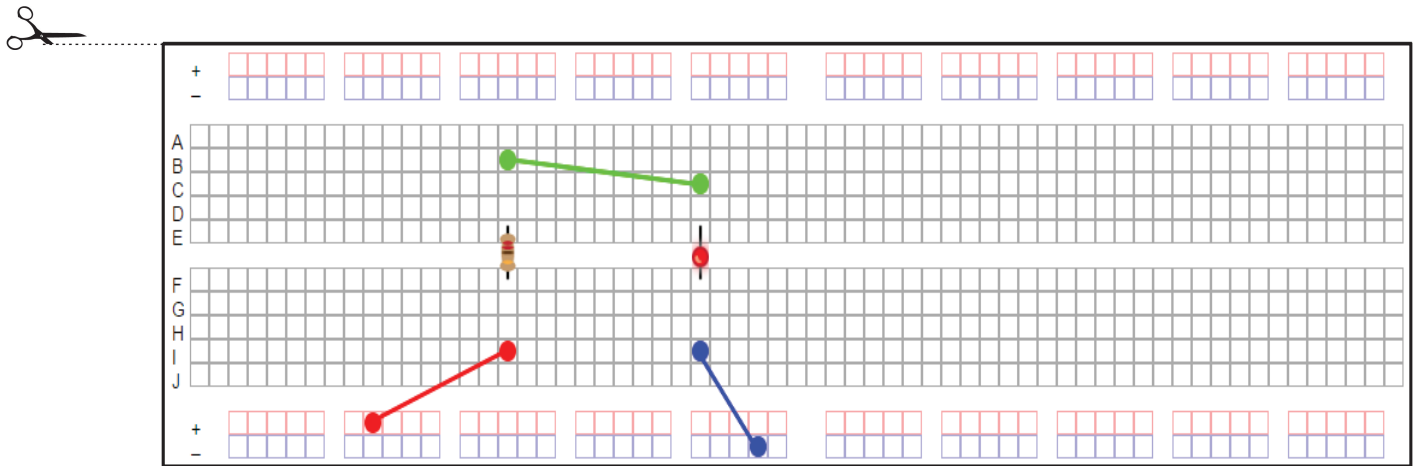


Paper Bread

An interactive electronics lesson plan builder for teachers
By Mark Brown in partnership with The Construct @ RIT

This goal of the lesson is to light up a red LED.
Please add 5V power/ground to bottom rows



Red Wire	-	x1
Green Wire	-	x1
Blue Wire	-	x1
330Ω Resistor	-	x1
Red LED	-	x1